


1. (RL -circuit) Given R, L and U , solve the current $i(t)$ from the equation


$$L \cdot i'(t) + R \cdot i(t) = u(t)$$

when $u(t) = U$ and $i(0) = 0$, and draw the graphs of the voltages

$$U_R = R \cdot i(t) \text{ and } U_L = L \cdot i'(t)$$

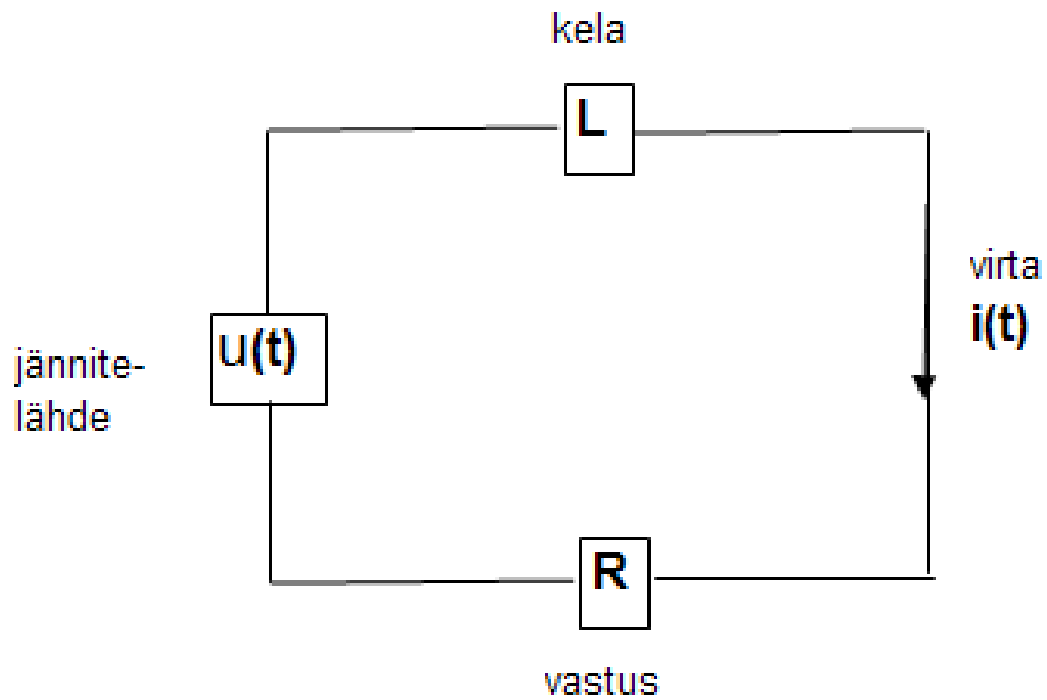on the interval $t = 0 \dots 5\tau$, where time constant $\tau = L/R$.




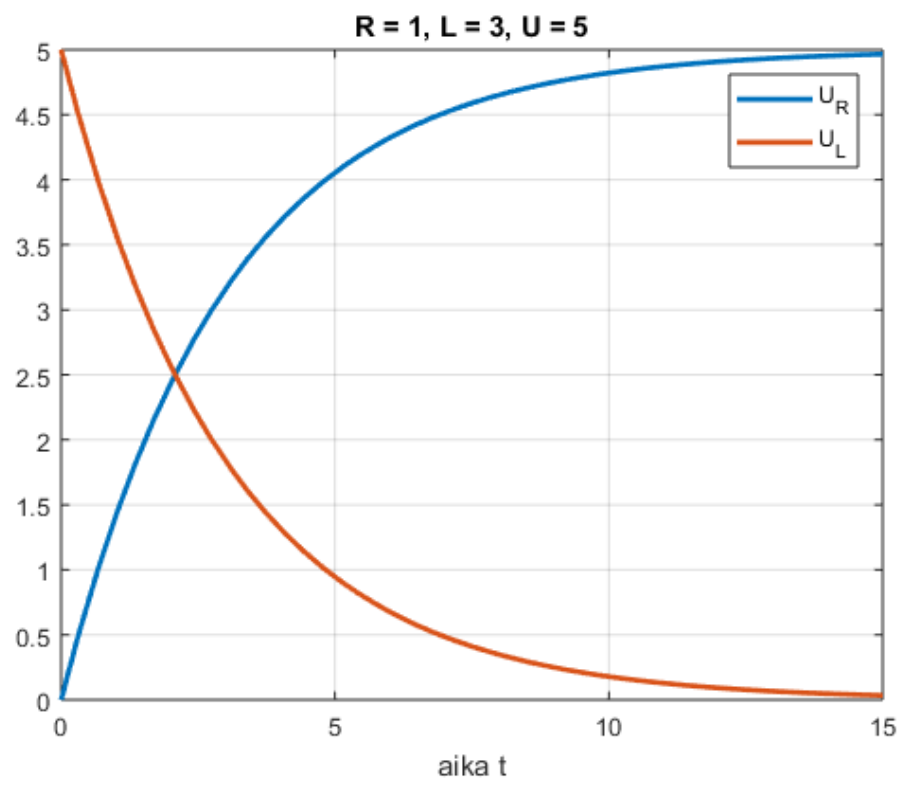

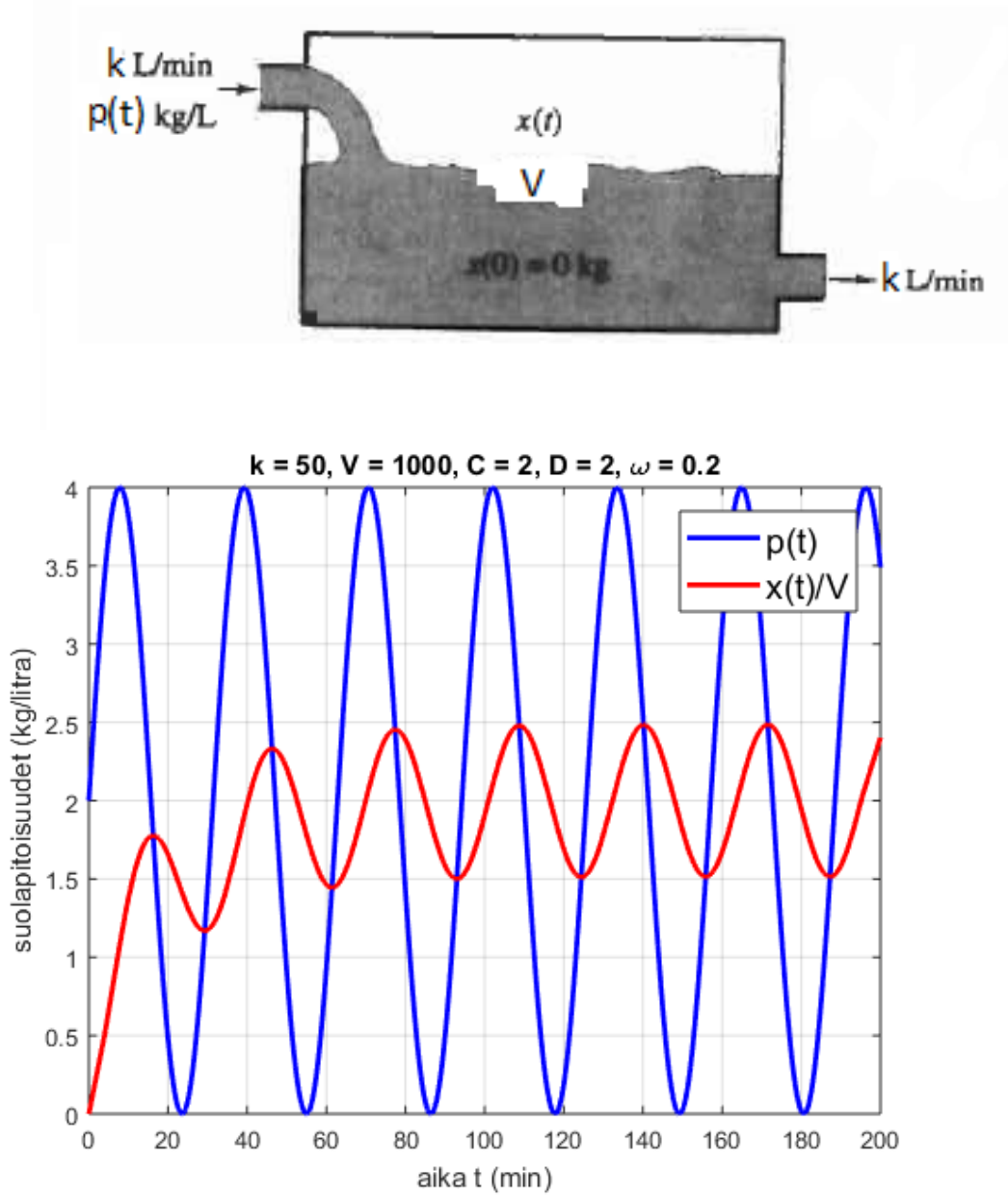2. Given the volume V (liters) of the tank, flow rate k (liters/min), amplitude C , constant D and angular frequency ω of the incoming salt content (kg/liter)

$$p(t) = C \sin(\omega t) + D$$


solve the mass $x(t)$ (kg) of the salt in the tank and draw the graphs of salt contents $x(t)/V$ and $p(t)$ on the interval $t = 0 \dots 10\tau$, where $\tau = V/k$



Deduce from the solution formulas that the salt content

$$\frac{x(t)}{V} \approx K \cdot C \sin(\omega t + \theta) + D, \text{ as } t \text{ increases}$$

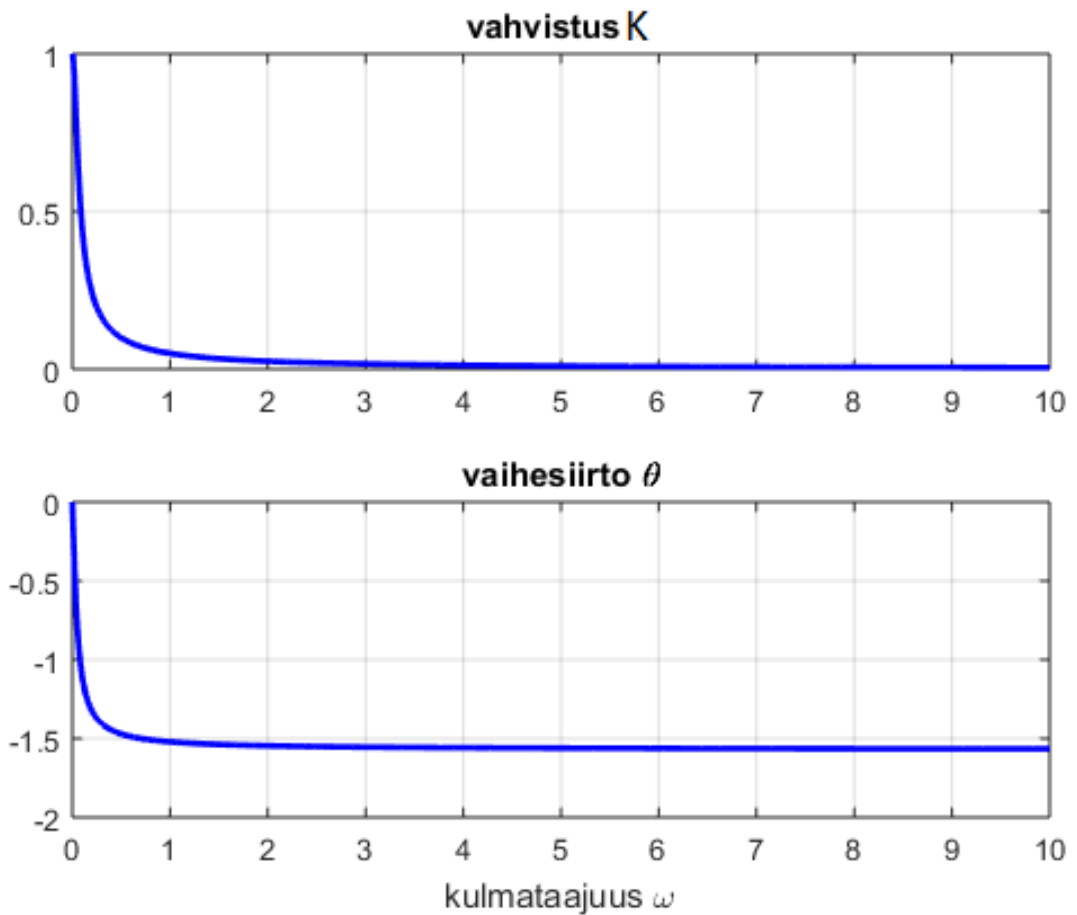and draw the graphs of the amplification K and phase shift θ on the interval $\omega = 0 \dots 100$




3. (*RLC*-circuit) Given R, L, C, U and T , solve $q(t)$ from the equation



$$L \cdot q''(t) + R \cdot q'(t) + \frac{1}{C} \cdot q(t) = U, \quad q(0) = 0, \quad q'(0) = 0$$

and draw the graphs of the voltages


$$U_R = R i(t), \quad U_L = L i'(t) \quad \text{and} \quad U_C = q(t)/C$$

on the interval $t = 0 \dots T$.

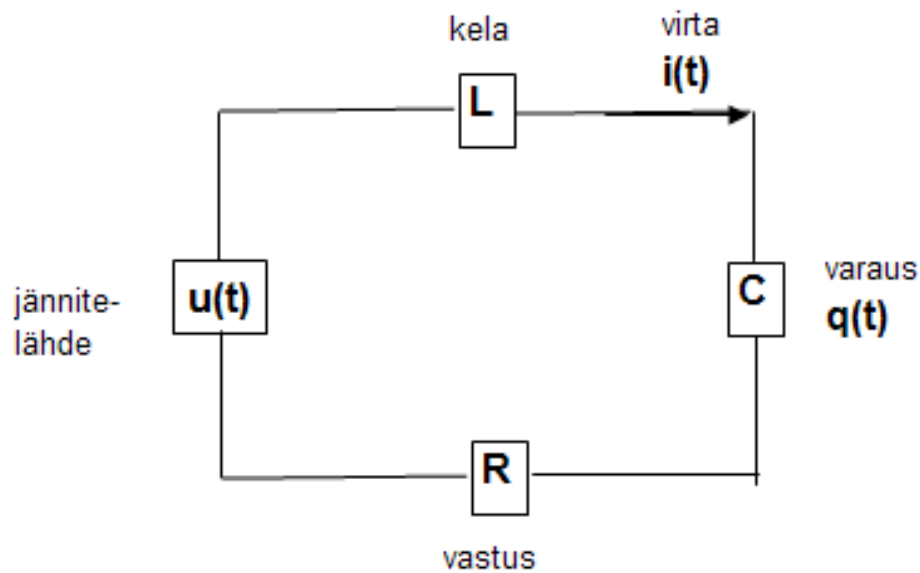

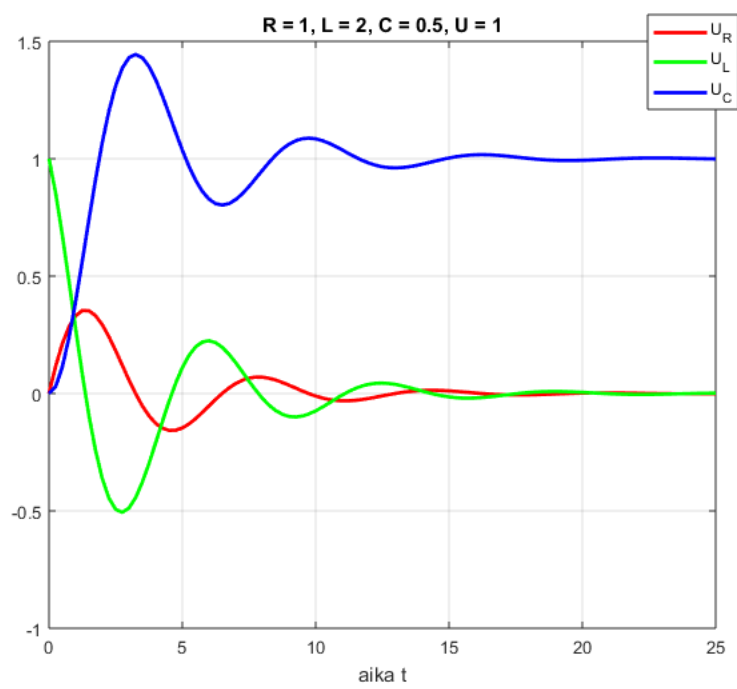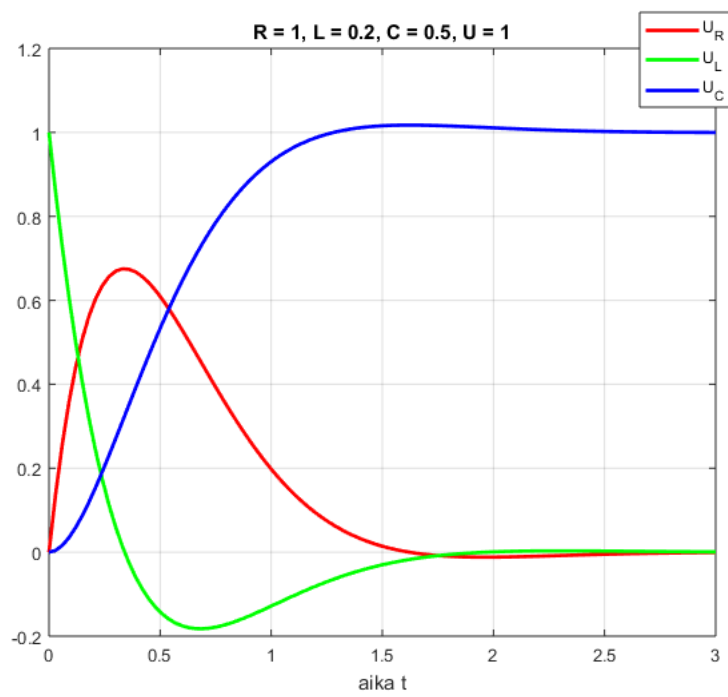


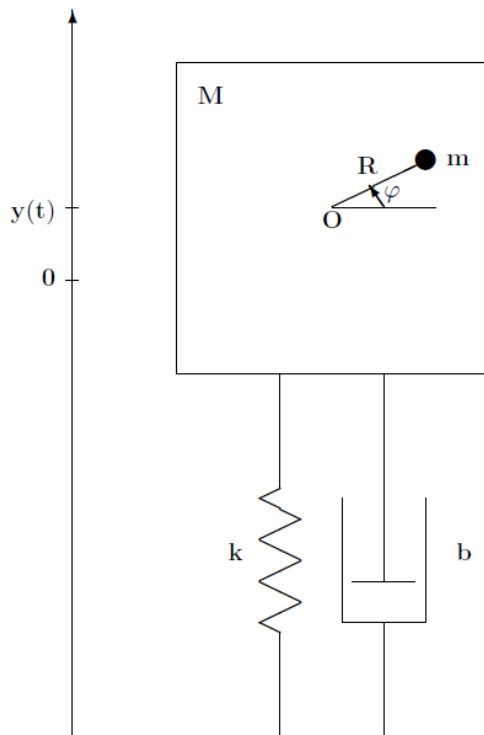
4. Mass m is rotating at angular speed ω (rad/sec), M is the total mass, $y(t)$ is the height of the center point O



Given M, m, k, b, R and ω , solve $y(t)$ from the equation

$$M y''(t) + b y'(t) + k y(t) = m R \omega^2 \sin(\omega t), \quad y(0) = 0, \quad y'(0) = 0$$

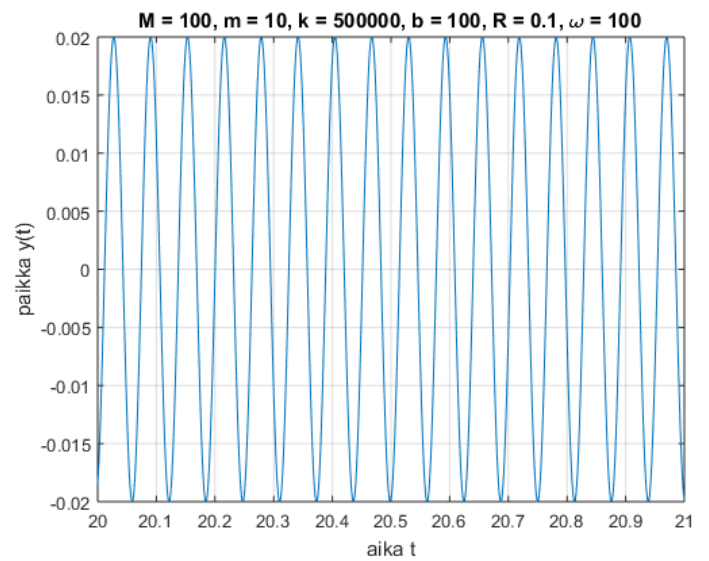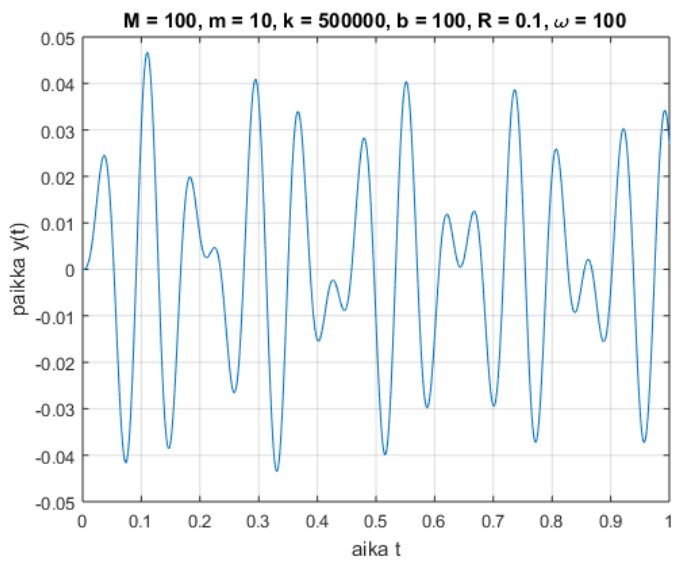
and draw it's graph (on a suitable interval of t).





Deduce from the solution formulas, that

$$y(t) \approx KA \sin(\omega t + \theta), \text{ as } t \text{ increases}$$

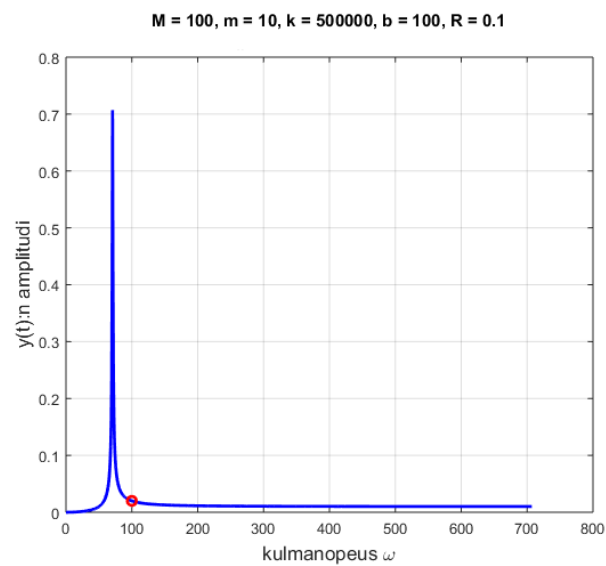and draw the graph of the amplitude KA on the interval $\omega = 0 \dots 10\sqrt{k/M}$



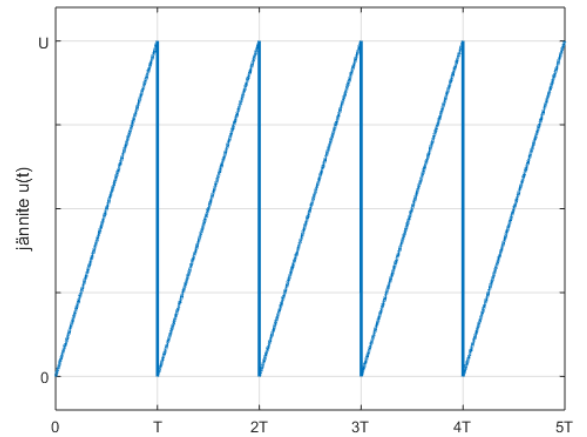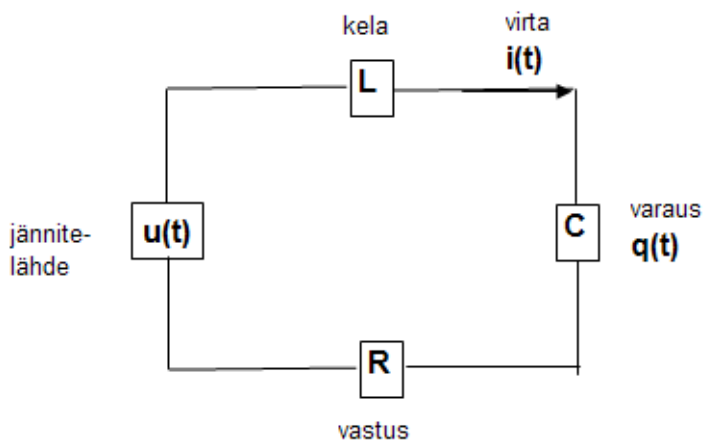5. RLC -circuit, input voltage $u(t)$ the saw tooth below





Given R, L, C, U and T , calculate the values of $q(t)$, $i(t) = q'(t)$ and $i'(t) = q''(t)$ numerically using the equation

$$L \cdot q''(t) + R \cdot q'(t) + \frac{1}{C} \cdot q(t) = u(t), \quad q(0) = 0, \quad q'(0) = 0$$

and draw the graphs of the voltages



$$U_R = R i(t), \quad U_L = L i'(t) \quad \text{ja} \quad U_C = q(t)/C$$

on the interval $t = 0 \dots 5T$

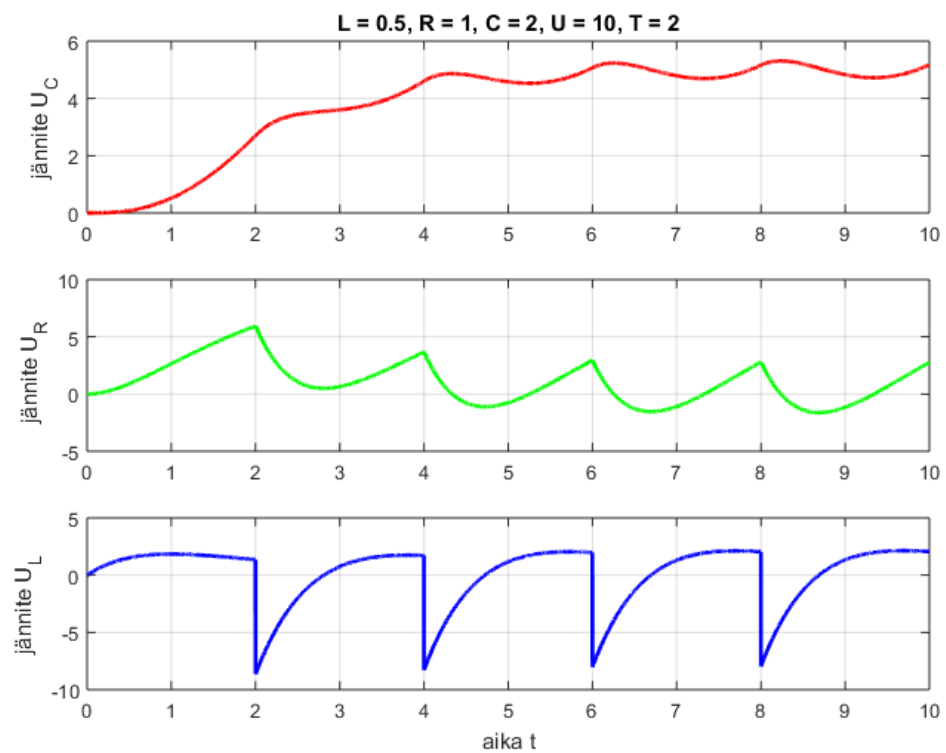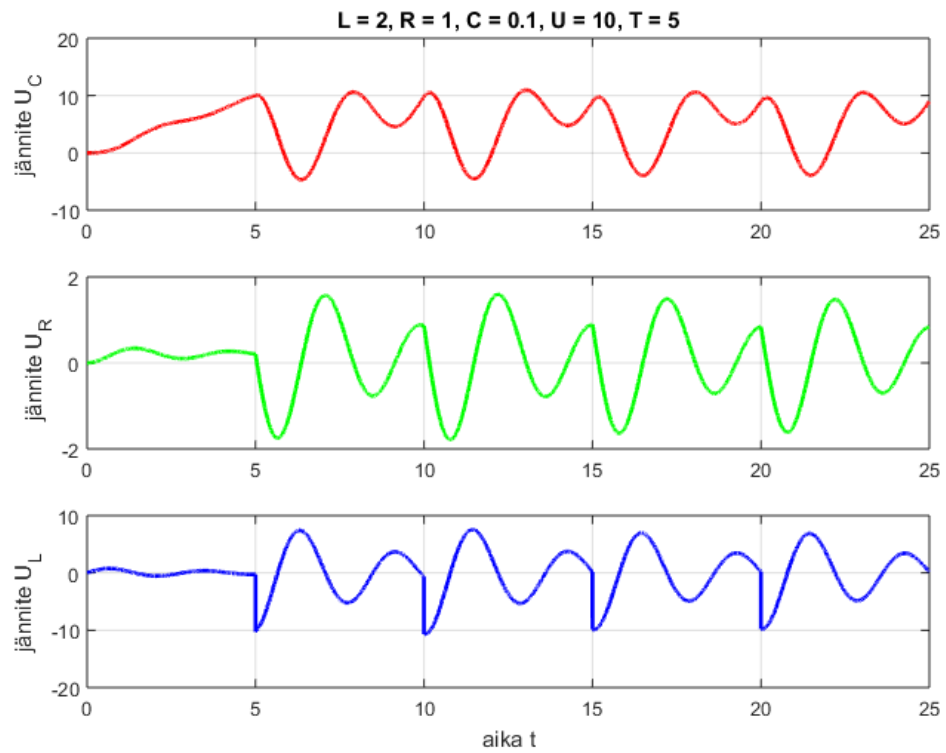

hint: ex 8

6. DC-motor

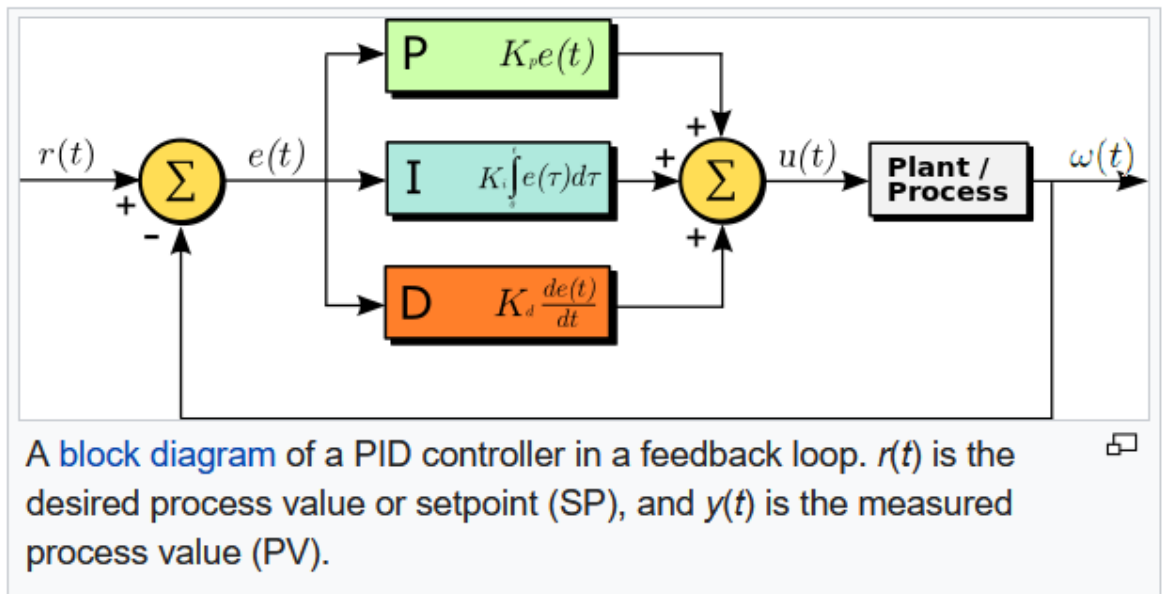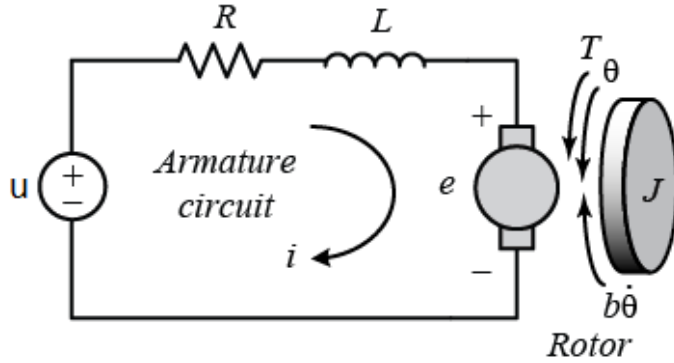

Given $J, L, R, b, K, K_p, K_i, K_d$, calculate the values of the PID-controlled angular speed $\omega(t)$ using the equation

$$JL\omega''(t) + (RJ + bL)\omega'(t) + (bR + K^2)\omega(t) = Ku(t)$$

$$\omega(0) = 0, \omega'(0) = 0$$

when setpoint $r(t) = 1$, and draw the graphs of $\omega(t)$, error $e(t) = r(t) - \omega(t)$ and the output $u(t)$ of the PID-controller

$$J = 0.1, L = 0.5, R = 0.3, b = 0.08, K = 0.1$$

$$K_p = 5, K_i = 2, K_d = 0.001$$

